

B.Sc. II Semester Examination 2021
Department of Computer Science, BHU
Paper code: CS-102: Digital Logic and Circuits


Time allotted: 1:30 hrs

Max. Marks: 20

Answer all questions

1. (a) $(2B)_{16} + (101)_8 + (101.2)_6 + (101101)_2 = (?)_3$ [1×5=5]
(b) Perform subtraction with the following binary number using 1's complement:
11010-11001
(c) Using 10's complement, subtract **31** from **43**.
(d) Implement the function $\Pi(0, 2, 4, 5)$ using NOR gates only.
(e) What is the largest 8 bit binary number? What is its Octal and Hexadecimal equivalent?

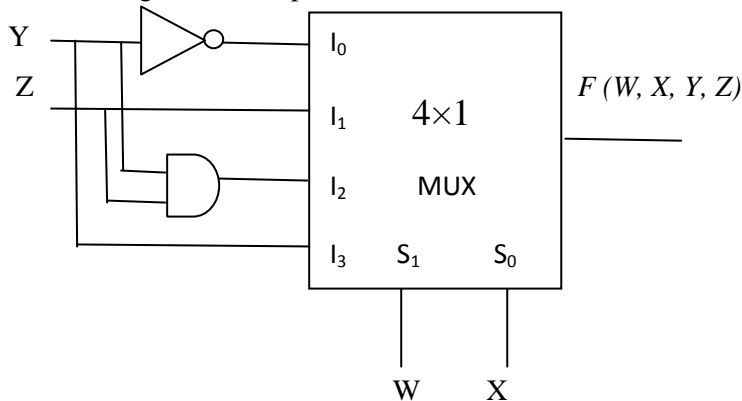-
2. Simplify the Boolean function $F = \sum m(0, 1, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11)$ using K-map. [4]
 3. The input to combinational logic circuit is a 4 bit binary number. Design the logic circuit with two outputs (Q1 and Q2) for the following conditions [5]
 - a. Q1=1 if the input binary number is 5 or less than 5.
 - b. Q2=0 if input number is 9 or more than 9.
 4. Consider the following 4×1 multiplexer: [3]



What is the Boolean function F in sum of minterms form?

5. A combinational circuit is defined by the functions $F_1(A, B, C) = \sum (1, 2, 4)$ and $F_2(A, B, C) = \sum (1, 3, 7)$. Implement the circuit using PLA. [3]

END
