

Application of Diode: Clippers & Clampers


BPT: 401: Electronics and Modern Physics

Tutorial – 8

Diode Clipper (Limiter):



Clippers or limiters is a type of diode network that has the ability to “clip off” a portion of the input ac signal without distorting the remaining part of the ac waveform.

Positive Clipping

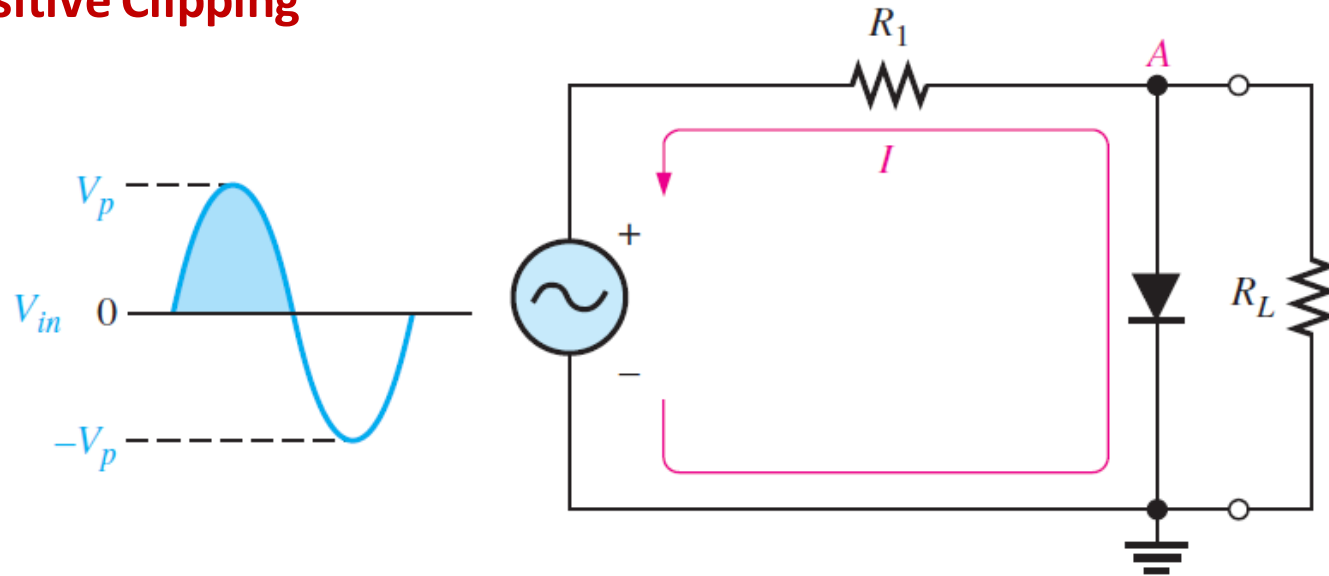

During the +ve half cycle:

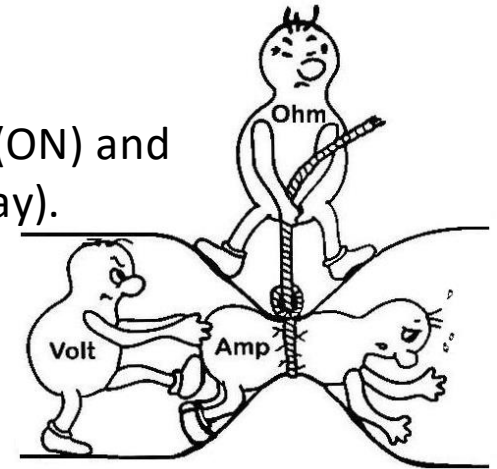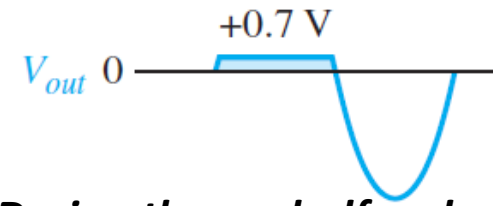
The Diode is forward biased (ON) and $V_{out} = V_D = 0.7 \text{ V}$ (Clipped away).



During the -ve half cycle:


The Diode is reverse biased (OFF) and $V_{out} = V_{in}$ (Remained).

Negative Clipping

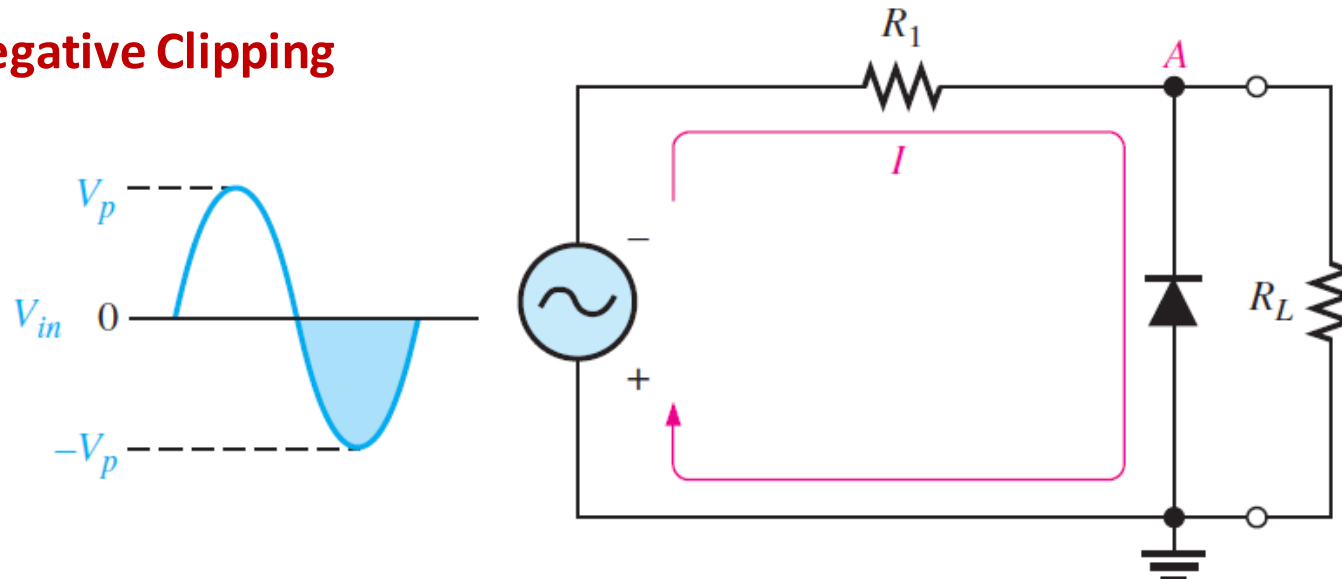

During the +ve half cycle:

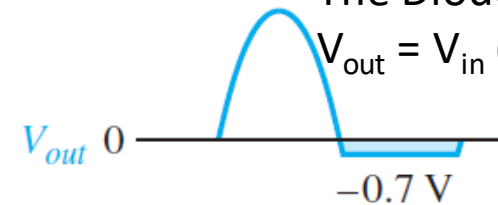The Diode is reverse biased (OFF) and $V_{out} = V_{in}$ (Remained).



During the -ve half cycle:


The Diode is forward biased (ON) and $V_{out} = V_D = 0.7 \text{ V}$ (Clipped away).

Diode Clipper (Limiter):


- ❖ In both Positive and Negative Clipping, a part of the output voltage looks like the input voltage.
- ❖ The output voltage is determined by the voltage divider formed by R_1 and the load resistor, R_L , as follows:

$$V_{out} = \frac{R_L}{R_1 + R_L} V_{in}$$

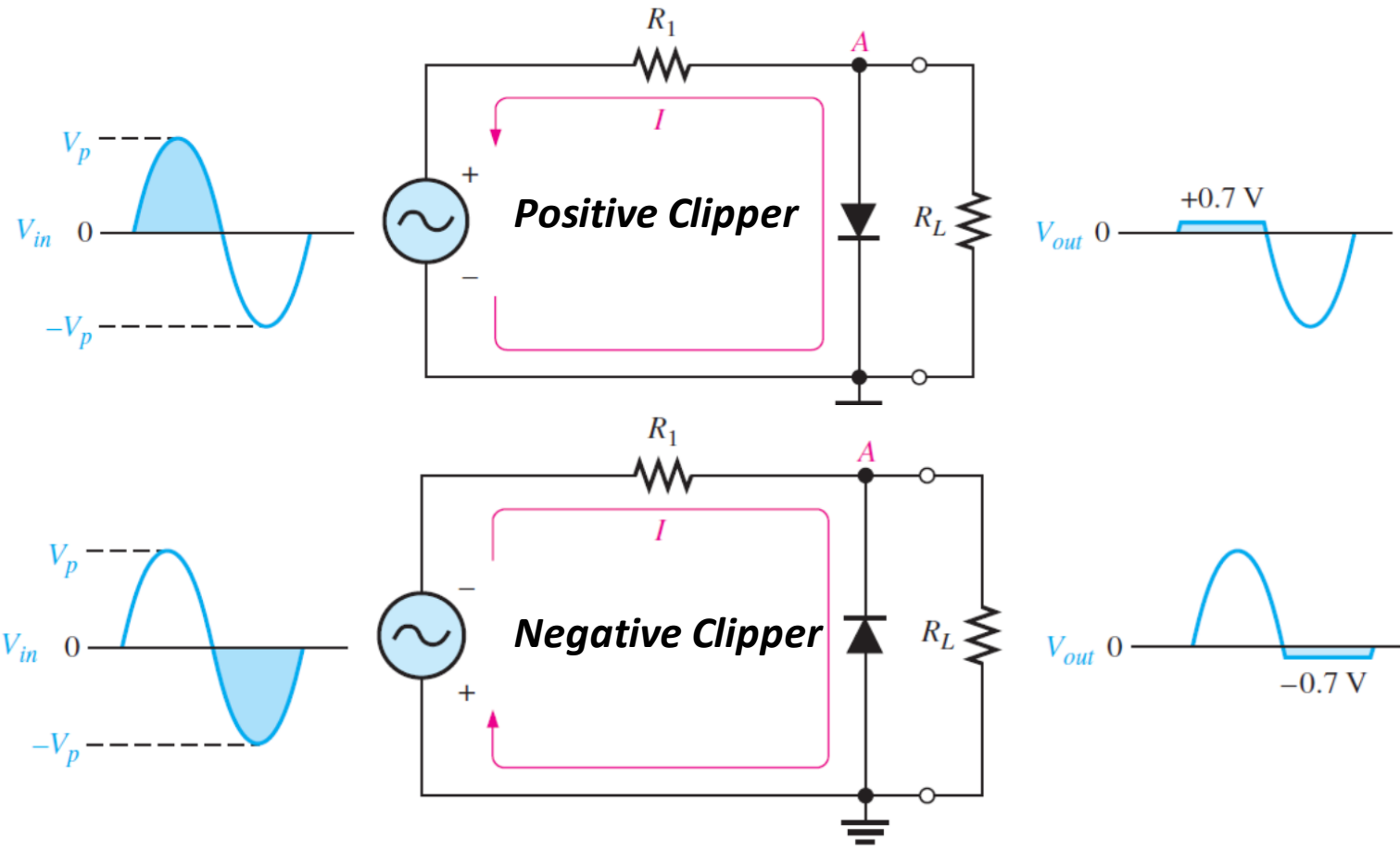- ❖ If R_1 is small compared to R_L , then $V_{out} = V_{in}$



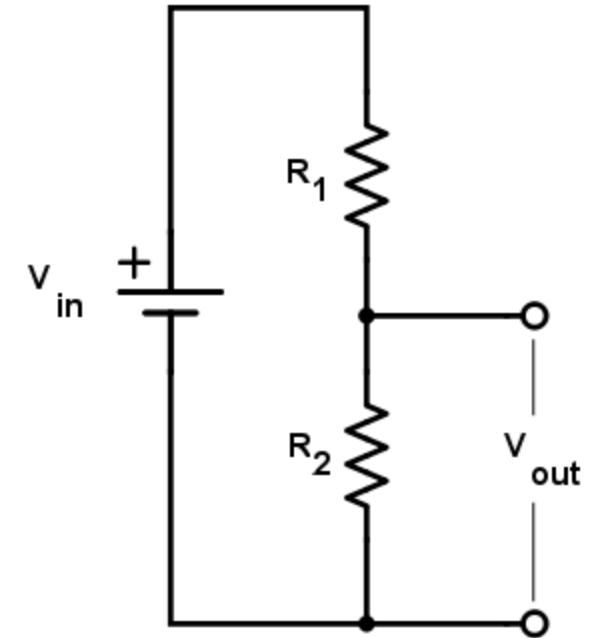Voltage divider or Potential divider Circuit




$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Biased Clipper


Biased Positive Clipper

- ❖ The level to which an ac voltage is clipped can be adjusted by adding a bias voltage, V_{BIAS} , in series with the diode.
- ❖ The voltage at point A must equal $V_{BIAS} + 0.7\text{ V}$ before the diode will become forward-biased and conduct.
- ❖ Once the diode begins to conduct, the voltage at point A is limited to $V_{BIAS} + 0.7\text{ V}$ so that all input voltage above this level is clipped off.

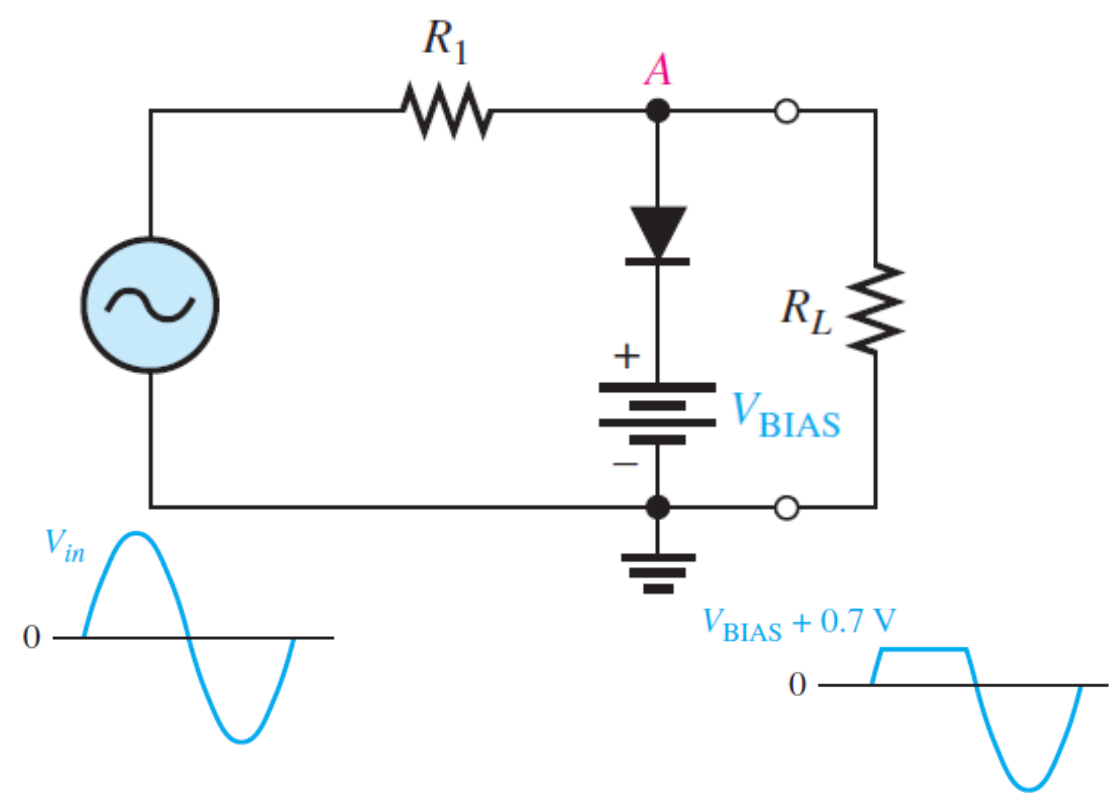


Biased Negative Clipper

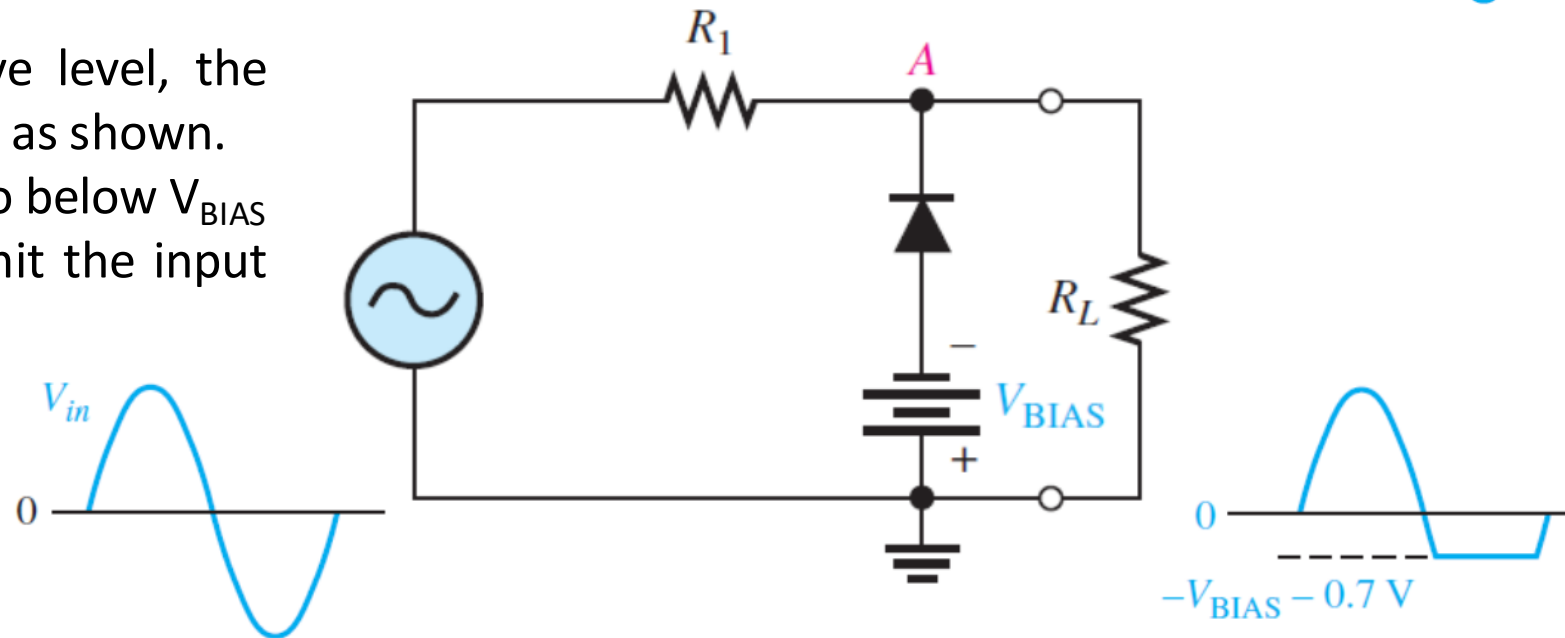- ❖ To limit a voltage to a specified negative level, the diode and bias voltage must be connected as shown.
- ❖ In this case, the voltage at point A must go below $V_{BIAS} - 0.7\text{ V}$ to forward-bias the diode and limit the input voltage.



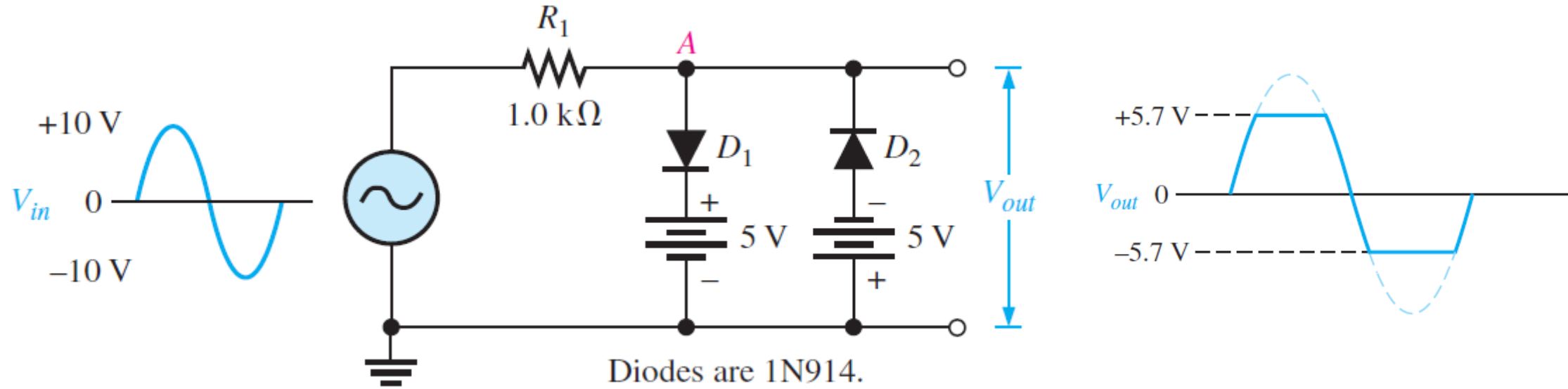Combination of Positive and Negative Clippers:





- ❖ When the voltage at point A reaches + 5.7 V (5 + 0.7), diode D_1 conducts and limits the output waveform to +5.7 V.
- ❖ Diode D_2 does not conduct until the voltage reaches - 5.7 V.
- ❖ Therefore, positive voltages above +5.7 V and negative voltages below - 5.7 V are clipped off
- ❖ It can be used for sinusoidal to square-wave conversion.

Diode Clamping Circuits


A clamper is a network constructed of a diode, a resistor and a capacitor that shifts the waveform to a different dc level without changing the appearance of the applied signal. In other words, adding dc voltage (V_C) to the ac signal.





Positive Clamping

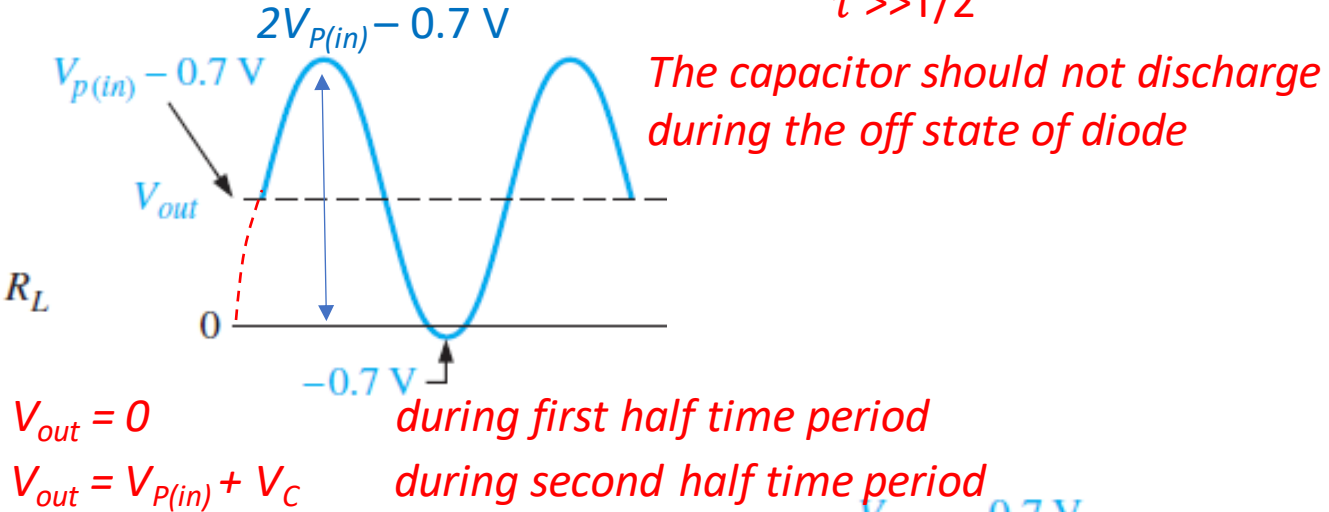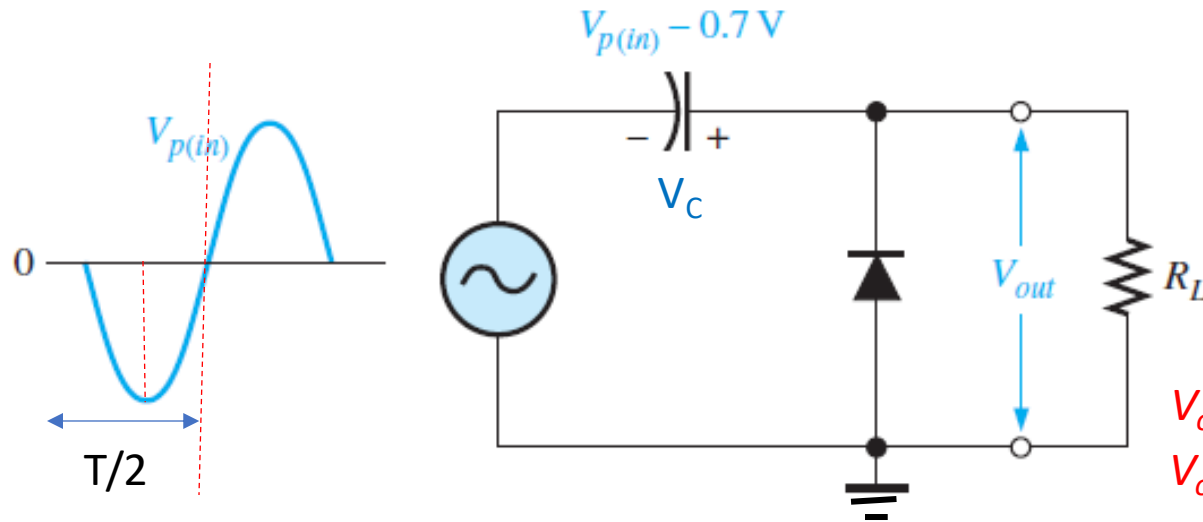A positive clamper adds a positive dc level to an ac voltage.



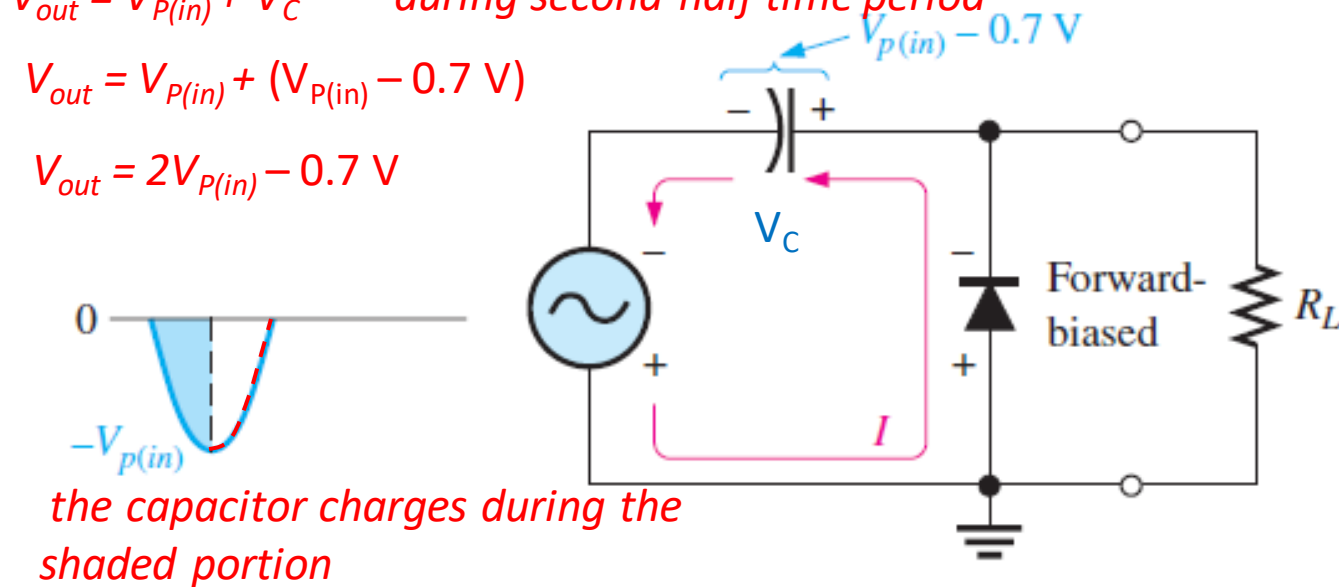- ❖ During the -Ve half cycle: the diode is forward biased, allowing the capacitor to charge to near the peak of the input
- ❖ During the +Ve half Cycle: the diode is reverse-biased. The capacitor can only discharge through the resistance of R_L .
- ❖ The amount that is discharged capacitor depends on the value of R_L .




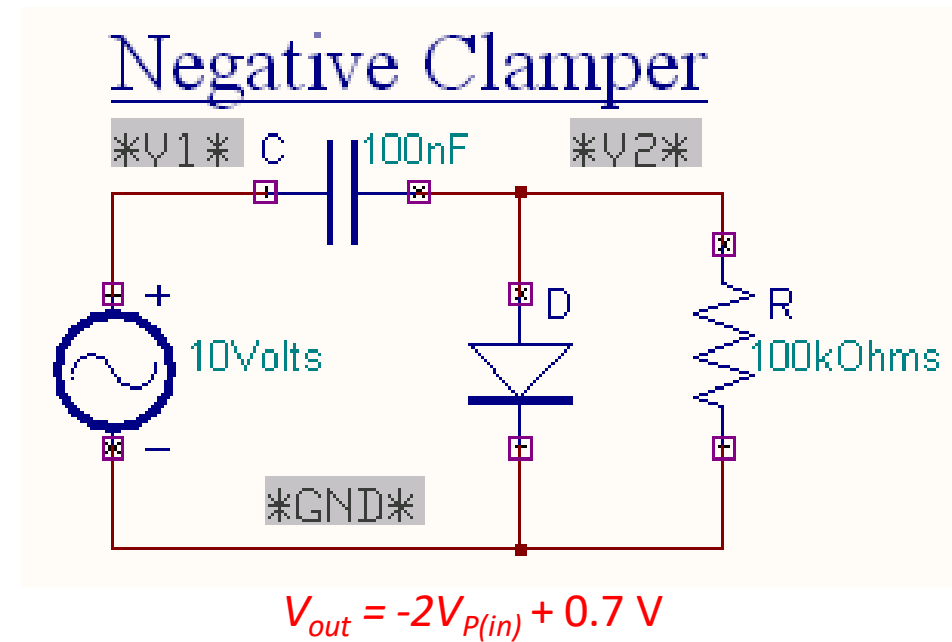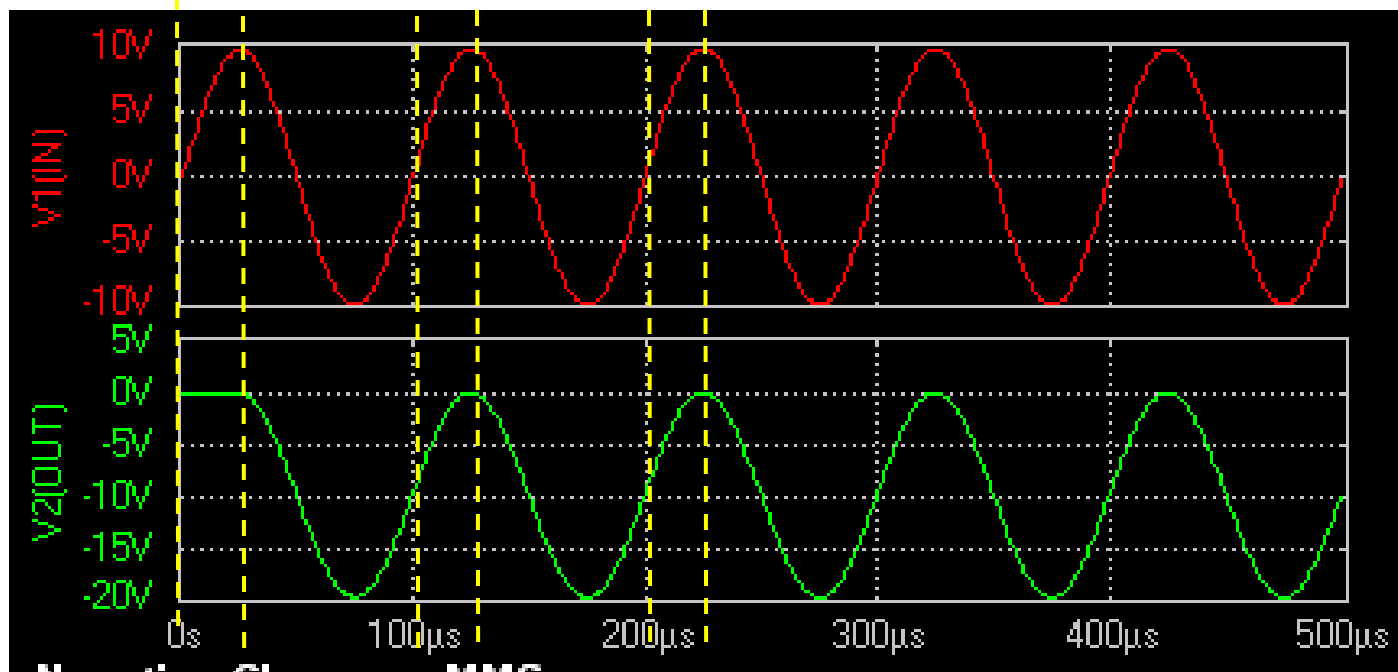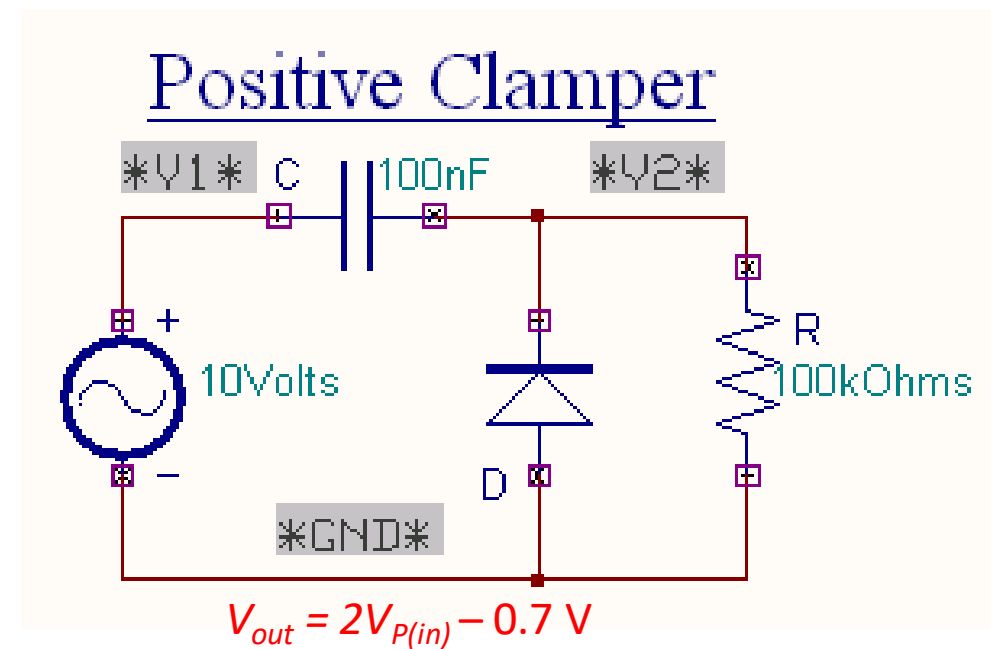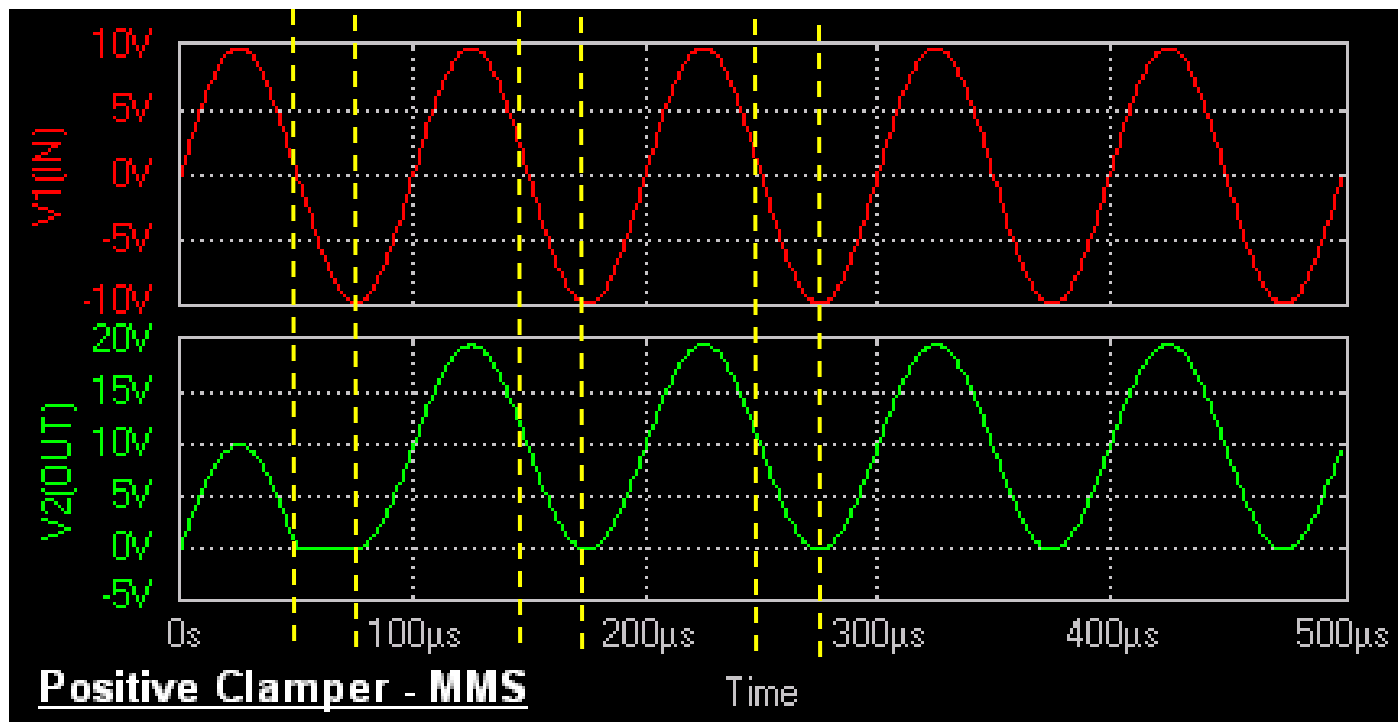

Diode Clamping Circuits

Negative Clamping

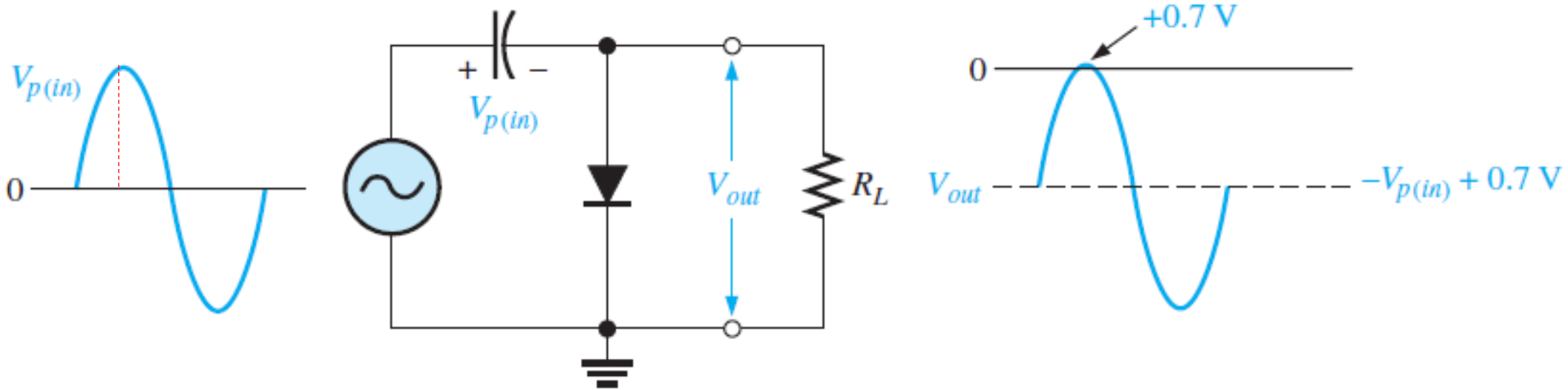A negative clamper adds a negative dc level to an ac voltage.



- ❖ During the +Ve half cycle: the diode is forward biased, allowing the capacitor to charge to near the peak of the input
- ❖ During the -Ve half Cycle: the diode is reverse-biased. The capacitor can only discharge through the resistance of R_L .
- ❖ The amount that is discharged capacitor depends on the value of R_L .