

# Digital Logic and Circuit

## Paper Code: CS-102

---

# Outline

---

## Combinational circuit

- **Code conversion**
- **Encoders & decoders**

# Code Converter

---

- The availability of a large variety of codes for the same discrete elements of information results in the use of different codes by different digital systems.
- It is sometimes necessary to use the output of one system as the input to another.
- A conversion circuit must be inserted between the two systems if each uses different codes for the same information.
- Thus, a code converter is a circuit that makes the two systems compatible even though each uses a different binary code.
- To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output lines must generate the corresponding bit combination of code B.
- A combinational circuit performs this transformation by means of logic gates.


# Conversion from the BCD to the excess-3 code.

---

- The bit combinations for the BCD and excess-3 codes are of 4 bit. Since each code uses four bits to represent a decimal digit, there must be four input variables and four output variables.
- Let us designate the four input binary variables by the symbols A, B , C, and D , and the four output variables by w, x, y, and z.
- The truth table relating the input and output variables is shown in Table.
- Note that four binary variables may have 16 bit combinations, only 10 of which are listed in the truth table.
- The six bit combinations not listed for the input variables are don't-care combinations.
- Since they will never occur, we are at liberty to assign to the output variables either a 1 or a 0, whichever gives a simpler circuit.

**Truth Table for Code-Conversion Example**


Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 

**Truth Table for Code-Conversion Example**

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 Maps for a BCD-to-excess-3-code converter



Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0


Maps for a BCD-to-excess-3-code converter

$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D' = B'(C + D) + B(C + D)'$$

$$w = A + BC + BD = A + B(C + D)$$

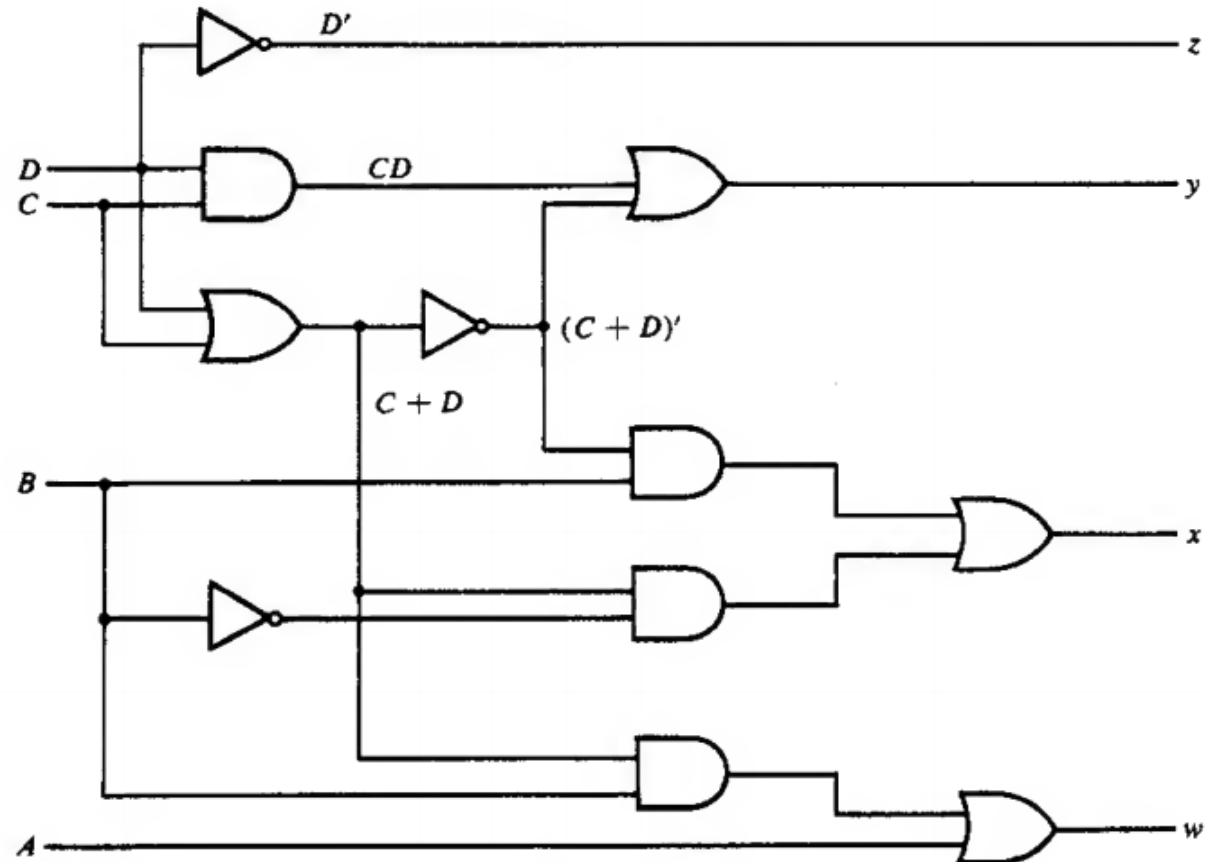

Logic diagram for a BCD-to-excess-3-code converter



# DECODERS

---


- A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.
- If the  $n$ -bit decoded information has unused or don't-care combinations, the decoder output will have fewer than  $2^n$  outputs.
- The decoders presented here are called  $n$ -to- $m$ -line decoders, where  $m \leq 2^n$ .
- Their purpose is to generate the  $2^n$  (or fewer) minterms of  $n$  input variables.
- The name decoder is also used in conjunction with some code converters such as a BCD-to-seven segment decoder.

- 
- As an example, consider the 3-to-8-line decoder circuit.
  - The three inputs are decoded into eight outputs, each output representing one of the minterms of the 3-input variables.
  - The three inverters provide the complement of the inputs, and each one of the eight AND gates generates one of the minterms.
  - A particular application of this decoder would be a binary-to-octal conversion.
  - The input variables may represent a binary number, and the outputs will then represent the eight digits in the octal number system.

# Truth Table of a 3-to-8-Line Decoder

---

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

# Encoder

---

- An encoder has  $2^n$  (or fewer) input lines and  $n$  output lines.
- The output lines generate the binary code corresponding to the input value.
- An example of an encoder is the octal to-binary encoder whose truth table is given in Table .
- It has eight inputs, one for each of the octal digits, and three outputs that generate the corresponding binary number.
- It is assumed that only one input has a value of 1 at any given time; otherwise the circuit has no meaning.

➤ The encoder can be implemented with OR gates whose inputs are determined directly from the truth table.

➤ Output z is equal to 1 when the input octal digit is 1 or 3 or 5 or 7.

➤ Output y is 1 for octal digits 2, 3, 6, or 7, and

➤ output x is 1 for digits 4, 5, 6, or 7. These conditions can be expressed by the following output Boolean functions:

$$z = D_1 + D_3 + D_5 + D_7$$


$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

# The encoder is implemented with three OR gates

---

 

Octal-to-binary encoder


# Multiplexer

---

- A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.



 - 
- A 4-to-1 -line multiplexer is shown in the Figure.
  - Each of the four input lines,  $I_0$  to  $I_3$ , is applied to one input of an AND gate.
  - Selection lines  $S_1$  and  $S_0$  are decoded to select a particular AND gate.




(a) Logic diagram

- 
- The function table lists the input-to-output path for each possible bit combination of the selection lines.

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 
(b) Function table

- When this MSI function is used in the design of a digital system, it is represented in block diagram form, as shown in Figure (c)



 (c) Block diagram

- To demonstrate the circuit operation, consider the case when  $S_1S_0 = 10$ .
- The AND gate associated with input  $I_2$  has two of its inputs equal to 1 and the third input connected to  $I_2$ .
- The other three AND gates have at least one input equal to 0, which makes their outputs equal to 0.
- The OR gate output is now equal to the value of  $I_2$ , thus providing a path from the selected input to the output.
- A multiplexer is also called a data selector, since it selects one of many inputs and steers the binary information to the output line. A multiplexer is often abbreviated as MUX.



(a) Logic diagram

# Suggested Reading

---

- M. Morris Mano, Digital Logic and Computer Design, PHI.

---

**Thank you**

