



**BYJU'S Classes**  
with **Two Teacher Advantage**

**Double the teachers. Double the learning.**

[Book a Free Class](#)

## Transistor As Amplifier

One of the key characteristics of a transistor is that it can be used as an amplifier. Transistors can act as amplifiers while they are functioning in the active region. If the transistor is correctly biased, the need for a transistor as an amplifier arises. A transistor can take in a very small input signal and amplify it. A transistor can take in a very small input signal at the base junction and release the amplified signal through the collector.

Transistor amplifiers are used frequently in RF (radio frequency communication), audio amplification, etc. In this lesson, we will learn how a transistor works as an amplifier.

### Common-Emitter Configuration


For a transistor to work as an amplifier, we usually use the common-emitter configuration. The figure below shows how the transistor is set up when it is connected in a circuit as an amplifier.



**BYJU'S**  
**National Aptitude**  
**Test 2021**

[Register Free](#)

**Upto 100% Scholarship**

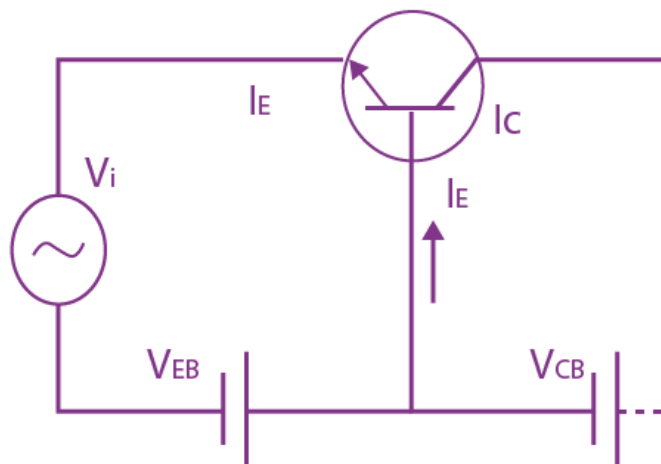


In the figure given above, the input is connected in forward-bias and the output is taken through the load in emitter-collector junction. There is also an application of DC voltage in the input circuit for amplification. Besides a small change in signal voltage results in the change of emitter current which is a large change in collector current due to the high resistance in the input circuit.
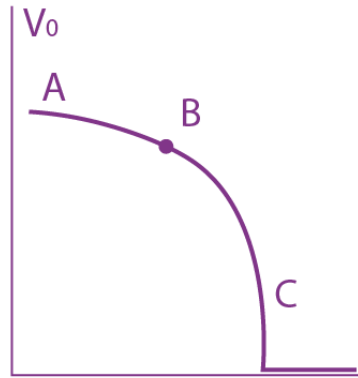
#### Also Read: [Forward Bias](#)


The output is taken across the load connected on the output side, which is a combination of R, L or C. The load resistance is of high value which causes a voltage drop. Overall, the weak signal is thus amplified in the collector circuit.

However, to work as an amplifier, the transistor has to work in the active region. The output voltage versus input voltage curve as seen in the figure below.



In the above graph, we have AB as the cut-off region, BC as the active region, and the region beyond C is the saturation region.

## Gain in Power, Current and Voltage

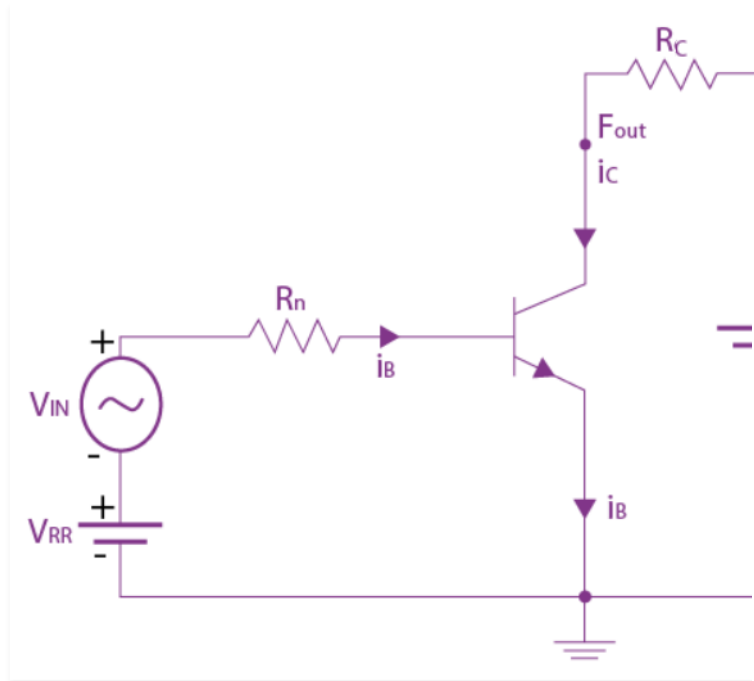

RV III'S

**JEE**  
Daily Quiz Videos  
[Click Here!](#)

The Learning App

START YOUR  
**JEE**  
PREPARATION  
[Buy Now](#)  
Classes 10, 11 & 12

From the figure that is given above it is clear that on the output side  $V_0$  is the output voltage,  $I_c$  is the collector current,  $R_c$  is the load resistance and  $V_0$  is the output voltage on the output side.

If we consider  $\Delta V_0$  and  $\Delta V_i$  as small changes in output and input voltage,  $\Delta V_0 / \Delta V_i$  is called as the small-signal voltage gain,  $A_v$  of the amplifier.

Therefore,  $\Delta V_0 = -R_c \Delta I_c$

The gain in terms of voltage when the changes in input and output are considered is called Voltage gain.

Similarly in input side,

$$V_{in} = I_B R_B + V_{BE}$$

Or

$$\Delta V_{in} = \Delta I_B R_B + \Delta V_{BE} \sim \Delta V_{in} = \Delta I_B R_B \quad (\Delta V_{BE} \ll \Delta I_B R_B)$$

Or,

$$A_v = \Delta V_0 / \Delta V_{in} = -R_c \Delta I_c / R_B \Delta I_B = -\beta_{ac} R_c / R_B$$

where  $\beta_{ac} = \Delta I_c / \Delta I_B$  is the AC current gain.

When there is gain in terms of current due to the changes in input current, it is called current gain.  $\beta$  value can range between 20 to 500.

Power gain of an amplifier is defined as the product of the current gain and voltage gain. It is also defined as the rate of change in output power.

Mathematically,  $A_p = \beta_{ac} \times A_v$

## Use of Capacitors

We have a coupling capacitor that is used to couple the AC component of the input signal of the amplifier. At the same time, the DC component will be invariantly present due to the amplifier.

## JEE Main and JEE Advanced Important Links

- JEE
- JEE Main
- JEE Main Exam Pattern
- JEE Main Syllabus
- JEE Main Eligibility Criteria
- JEE Main Answer Key
- JEE Main Question Paper
- JEE Main Question Paper Analysis
- JEE Main Sample Papers
- JEE Main Mock Test

being removed by the coupling capacitor at the output and hence signal being supplied to the load connected at the output.

**Also Read:** [Capacitor Types and Capacitance](#)

Similarly, we do have an Emitter- bypass Capacitor  $C_E$ . When AC amplifier circuit, the variable current will flow through resistors  $R_C$  and emitter, i.e.,  $R_C$  and  $R_E$ . This current in  $R_E$  will develop a variable voltage and provides additional negative feedback to the emitter junction.

This will result in an overall reduction of voltage gain associated with capacitor  $C_E$  connected across  $R_E$  provides a short circuit path for AC and reduce the effect of additional negative feedback due to the AC reduction in voltage gain.

## Role of Resistance

The resistors  $R_1$  and  $R_2$  form the voltage division circuit to supply base of the transistor. The resistors  $R_C$  and  $R_E$  control the collector and emitter currents respectively. Proper selection of these resistors helps us to control the currents. These resistors provide the required junction voltages and currents  $I_E$ ,  $I_B$  and  $I_C$  to work the transistor in the active region of operation.

The emitter resistor  $R_E$  produces the following changes in the performance of the amplifier.

- It causes bias stabilization
- It causes current gain to remain essentially unaltered.
- Increases the input and output impedances.
- It stabilizes the voltage gain.

**Also Read:** [Transformer](#)

## The Need for CE Configuration

We usually employ CE configuration for transistors as amplifiers because of its high values of current gain, voltage gain and power gain. Moreover, the

- JEE Main Crash Course
- JEE Advanced
- JEE Advanced Eligibility Criteria
- JEE Advanced Registration
- JEE Advanced Syllabus
- JEE Advanced Crash Course
- JEE Advanced Exam Answer Keys
- JEE Advanced Paper Analysis
- JEE Advanced Previous Year Papers
- JEE Advanced Sample Papers



degrees between input and output. It implies the output signal is an inverted version of the signal given in the input.

As we come to the end of the lesson, we have to know and remember that an amplifier in order to function properly must have the following characteristics:

- High input impedance.
- High gain.
- High slew rate.
- High bandwidth.
- High efficiency.
- High stability.
- High linearity.

## Solved Problems

**1. Consider a CE- transistor made to work as an amplifier. The voltage across the collector resistance of  $2\text{ K}\Omega$  is 2 volts. Suppose the  $\beta_{ac}$  factor of the transistor is 100 and base resistance is  $1\text{ K}\Omega$ , determine the base voltage and base current?**

**Answer:**

Given  $R_C = 2\text{ K}\Omega = 2000\text{ }\Omega$ ;  $V_C = 2\text{ V}$ ;  $\beta_{ac} = 100$ ;  $R_B = 1\text{ K}\Omega = 1000\text{ }\Omega$

Collector current,  $I_C = V_C/R_C = 2/2000 = 1\text{ mA}$

$I_B = V_B/R_B = V_B/1000 = V_B\text{ mA}$

$\beta_{ac} = 100 = I_C/I_B = 1/V_B$

$V_B = 1/100 = 0.01\text{ V}$

Therefore,  $I_B = V_B\text{ mA} = 0.01 / 1000 = 10 \times 10^{-6}\text{ A} = 10\text{ }\mu\text{A}$ .

**2. 2 amplifiers are connected in a series (cascaded). The voltage gain of the first amplifier is 10 and the second has 20 voltage gain. The input signal is given as 0.01 V.**

## Join BYJU'S Learning Program


Calculate the output of the AC signal?

Answer:

Total voltage gain is  $A_V = A_{V1} * A_{V2} = \Delta V_o / \Delta V_i$

$\Delta V_o = \Delta V_i * A_{V1} * A_{V2} = 0.01 * 10 * 20 = 2V$
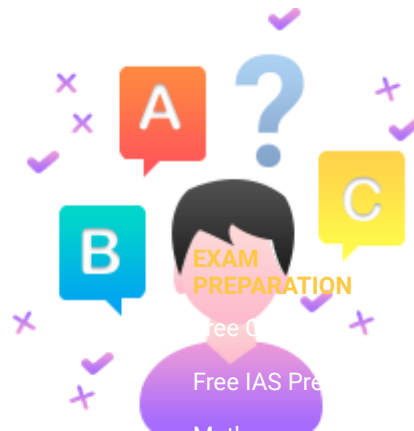
## ! Test Your Knowledge On Transistor As Amplifier!



Put your understanding of this concept to test by answering a few MCQs. Click 'Start Quiz' to begin!

Select the correct answer and click on the "Finish" button  
Check your score and answers at the end of the quiz

CLASSES

EXAMS

COMPANY

FREE TEXTBOOK SOLUTIONS

COURSES

3rd

5th

Home Tuition  
**Start Quiz**  
All Products

**FOLLOW US**



## STATE BOARDS

[Maharashtra](#) | [Gujarat](#) | [Tamil Nadu](#) | [Karnataka](#) | [Kerala](#) | [Andhra Pradesh](#) | [Telangana](#) | [Uttar Pradesh](#) | [Bihar](#) | [Rajasthan](#)  
[Madhya Pradesh](#) | [West Bengal](#)

[Disclaimer](#) | [Privacy Policy](#) | [Terms of Services](#) | [Sitemap](#)

© 2021, BYJU'S. All rights reserved.